

# Design of 4-bit Adder and Subtractor circuits using a ripple carry logic and carry look-ahead logic.

By:

James Feng Wu

Adam Harris

# Problem statement:

Our groups was to:

1. Design a 4-bit adder circuits using a ripple carry logic and carry look-ahead logic and
2. Design a 4-bit subtraction circuit using ripple carry logic

# Design goals

1. Optimize the design to implement the function using the smallest number of gate count.
2. Find the worst case gate delay in implementing the two adder designs.
3. Compare the two designs and summarize the results.

# Implementation

1. Implement the whole design in Mentor Graphics using Schematic capture tool suite.
2. Simulate the two design using the input stimulus list provided

# Full Adder

-A Full Adder is a circuit that adds two binary values with respect to the Carry Input. A full subtractor is just a Full Adder with certain inputs complemented

The formula for a full adder is  $X \oplus Y \oplus \text{Carry in}$ .



# Ripple Carry

-A ripple carry circuit can be thought of as serial data processing. Once an action is done, it is carried to the next stage. This is somewhat slower than other methods.


# Carry Look-Ahead

-Carry Look-Ahead logic can be thought of as parallel data processing. It does the same thing that the Ripple Carry does, but it does it all at the same time.

With the project requirements taken care of, Our team decided to add extra capabilities to our designs.
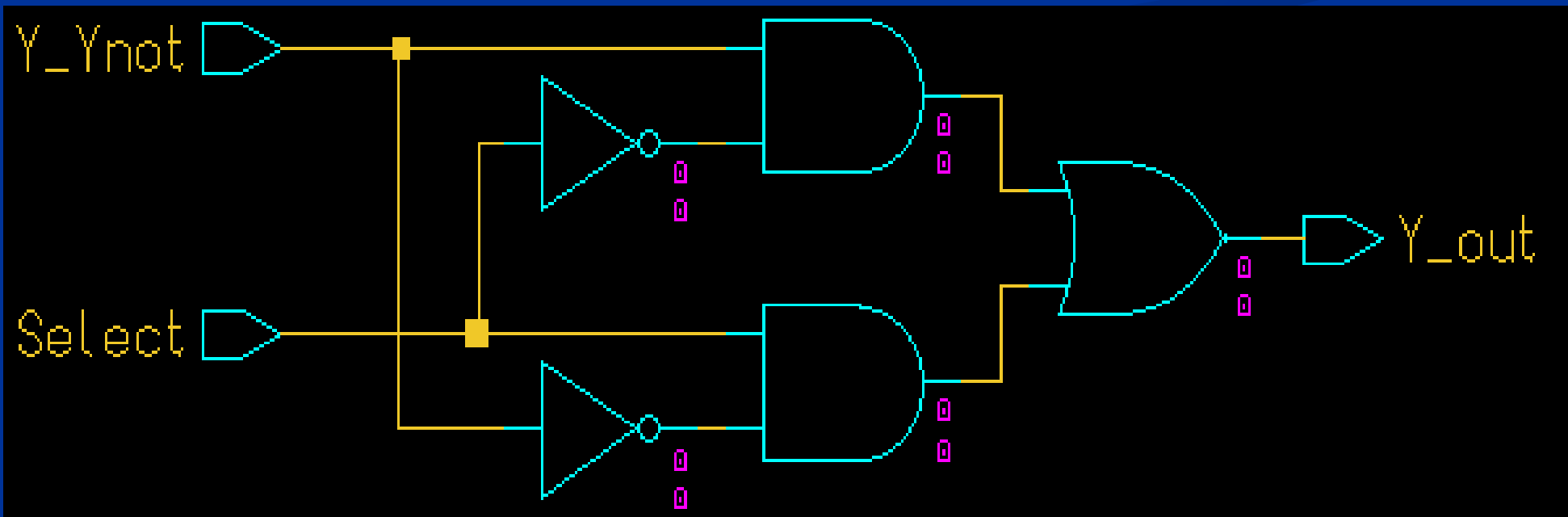
# Multiplexer

A multiplexer selects one of the input signals to be propagated to the output.




# Multiplexer

This allows the team to combine  
our Ripple Carry Adder and  
Ripple Carry Subtractor circuits.

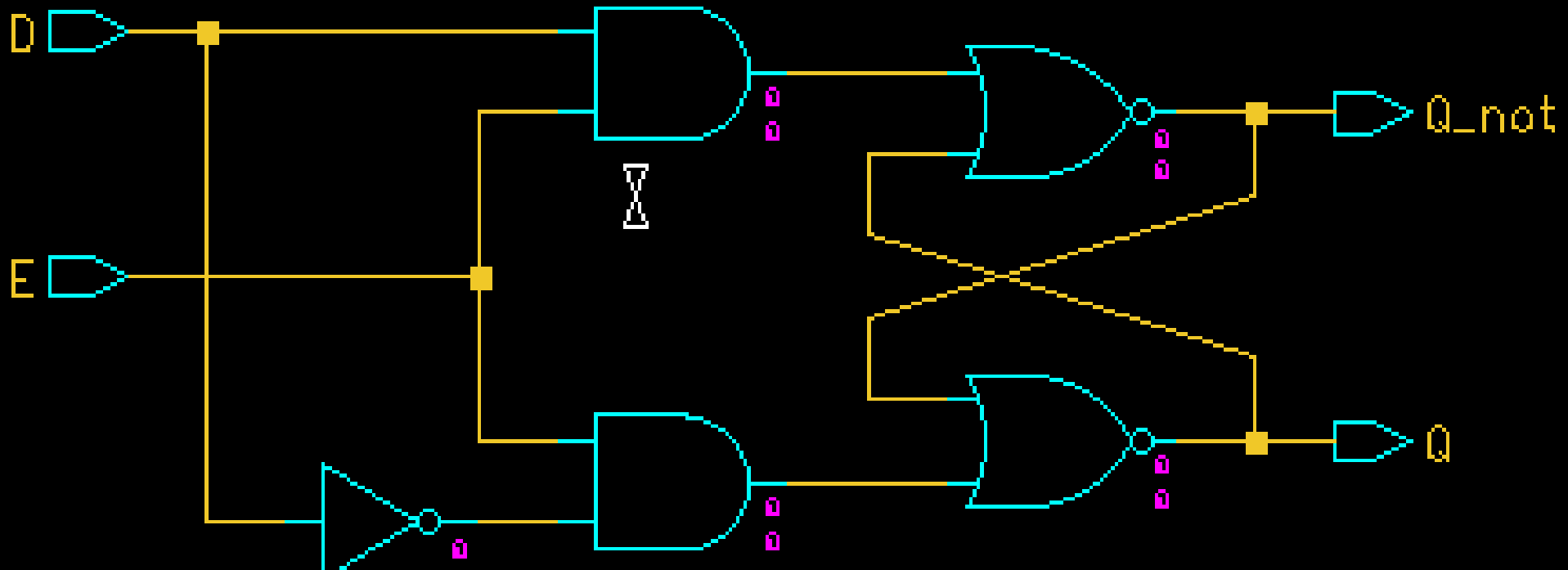
# D-Latch


A D-Latch is a memory storage circuit. It holds a value until the Enable pin is reset, this allows for an optional addition to the circuit which is a simple user interface.



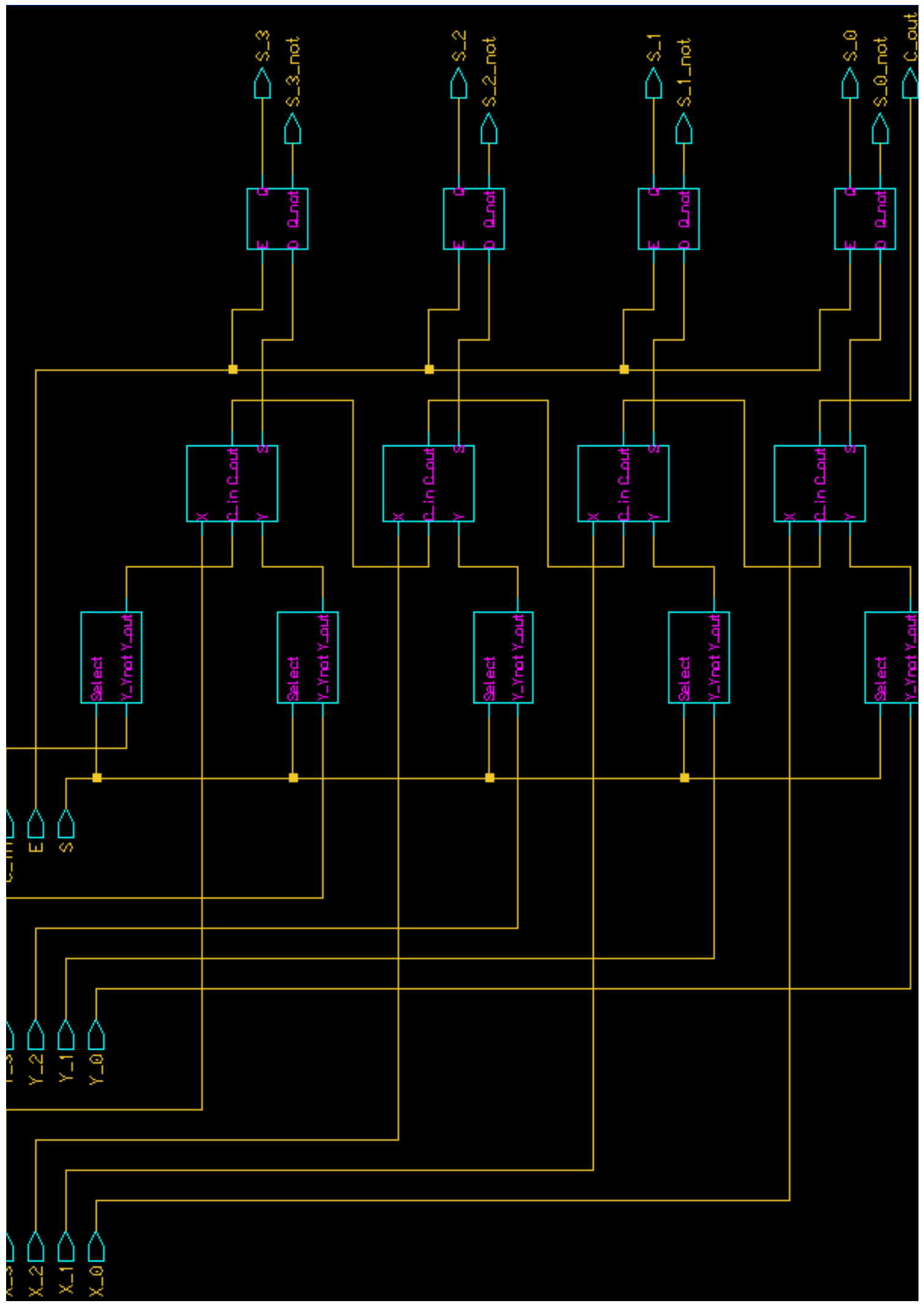
# Final Products


The final products are a Ripple Carry Full Subtractor/Subtractor with memory (for a simple user interface that may be added later if desired,) and a Carry Look-Ahead Full Adder.



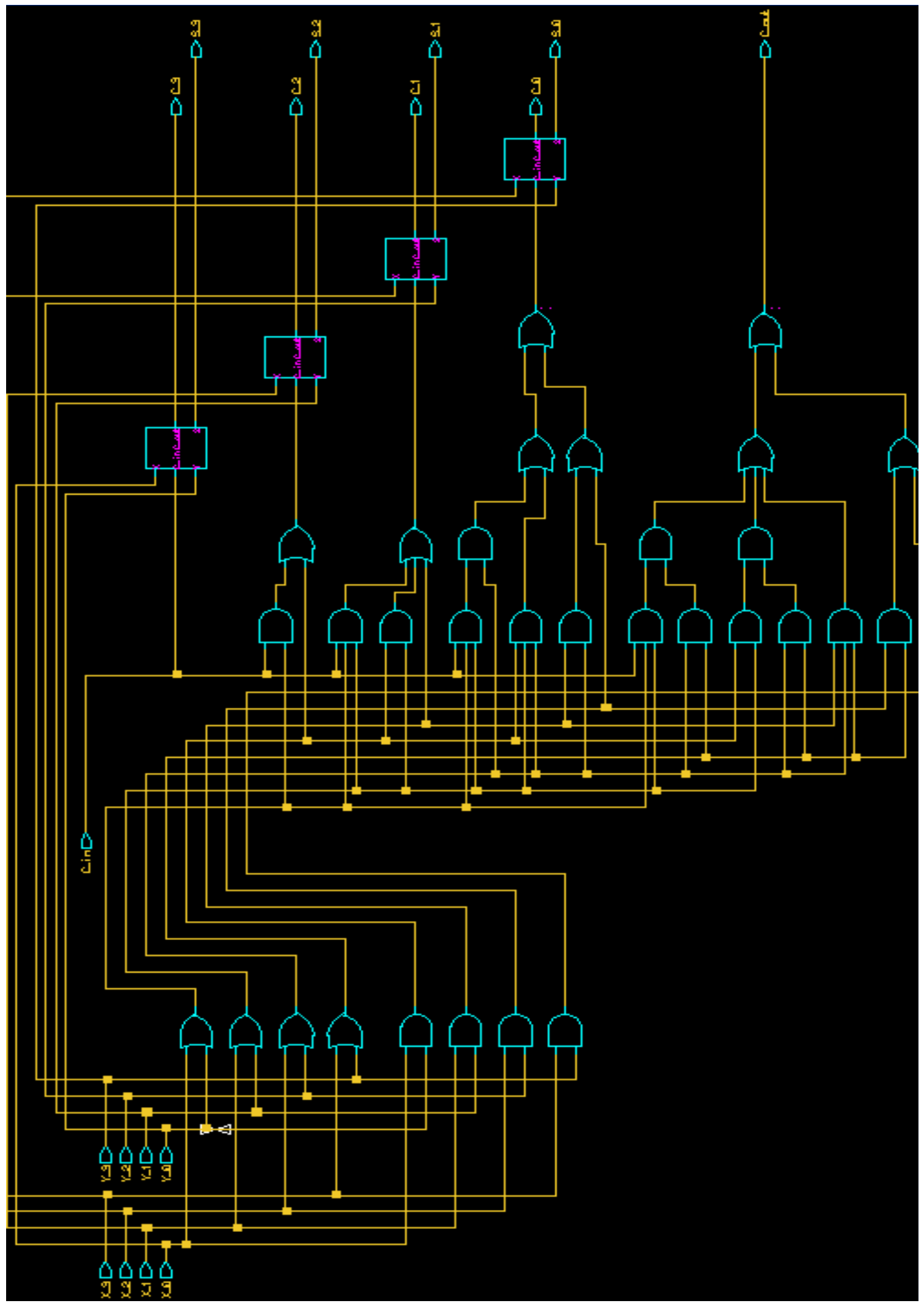



Outputs for the adders

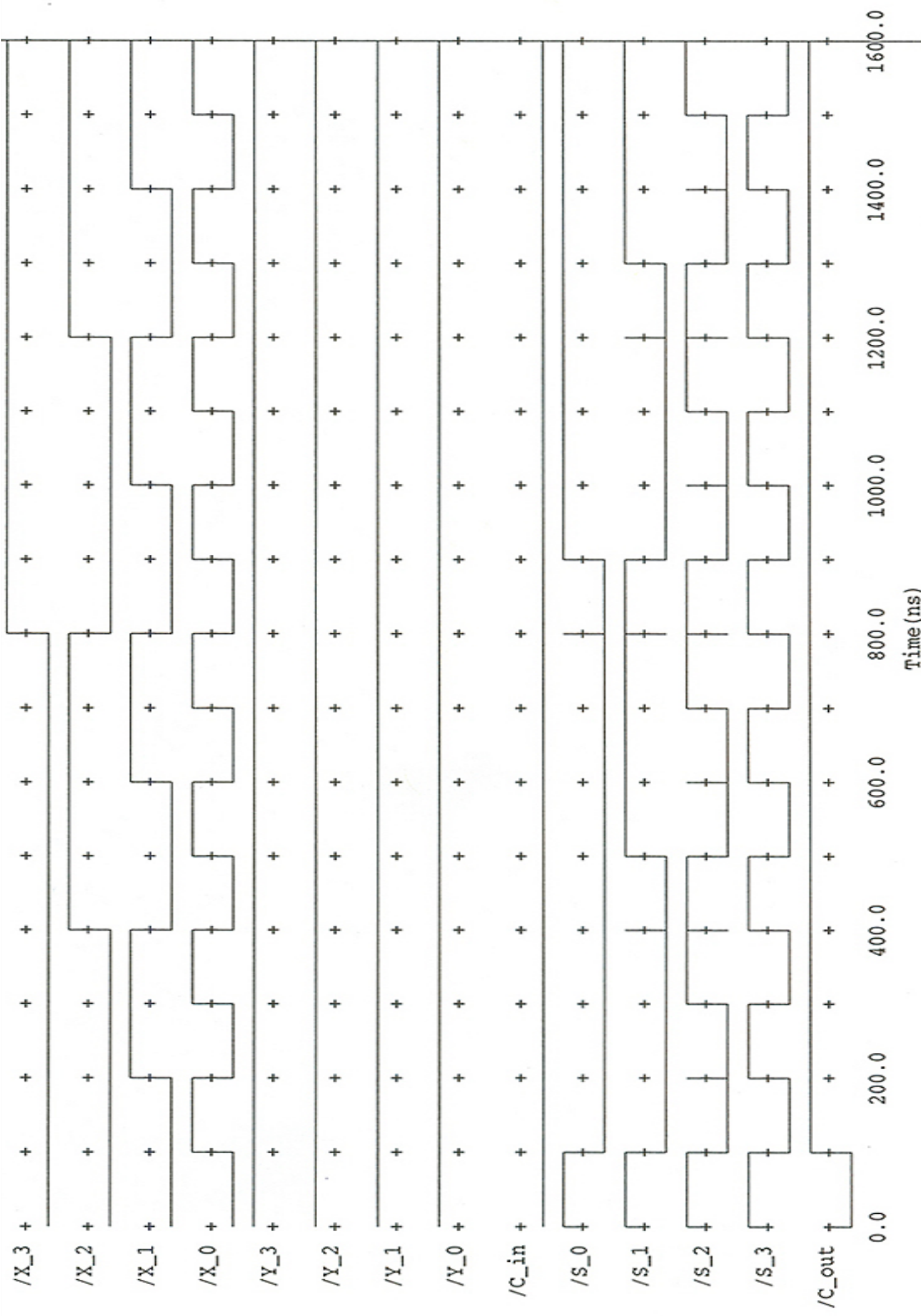

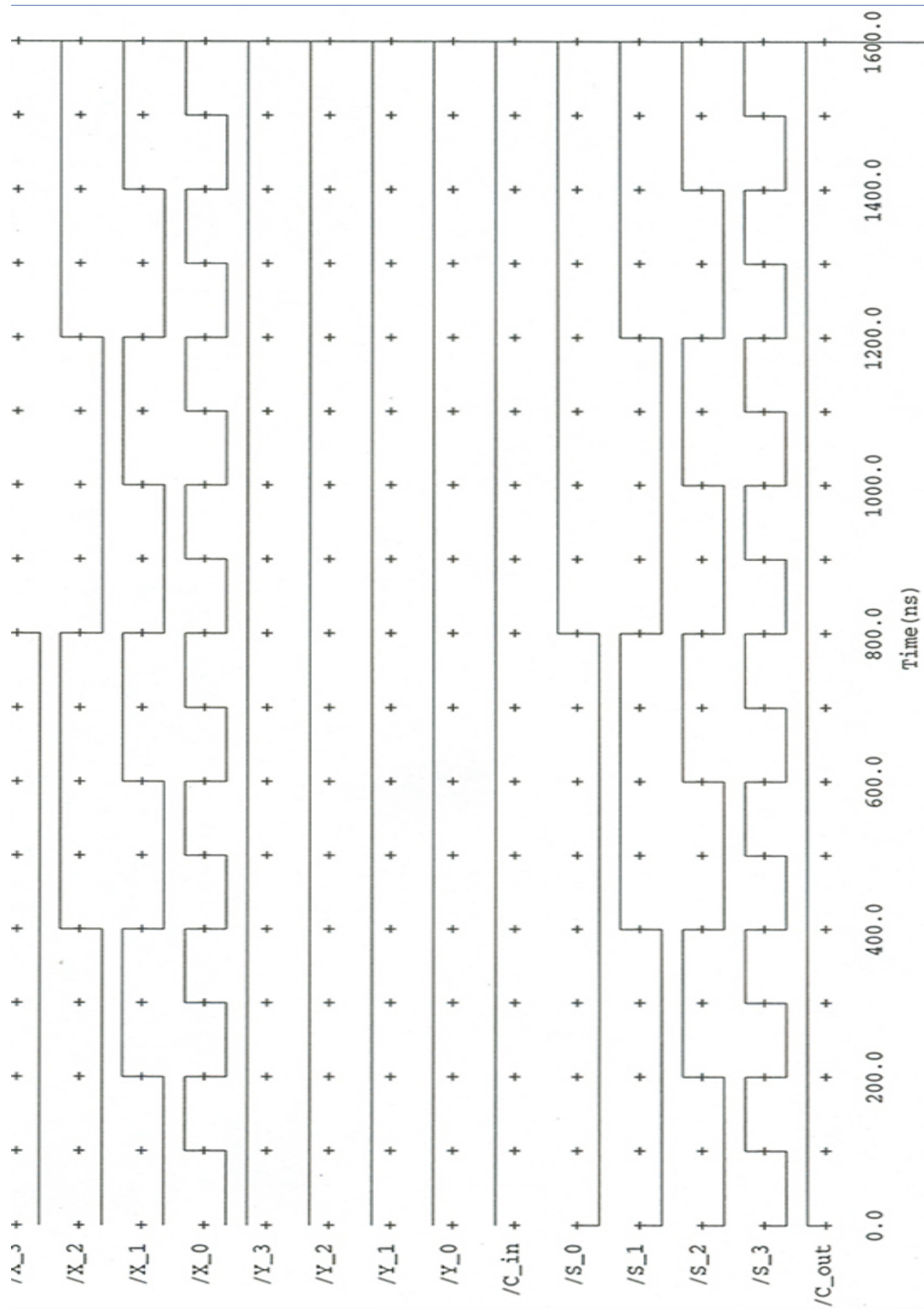

Outputs for the subtracter

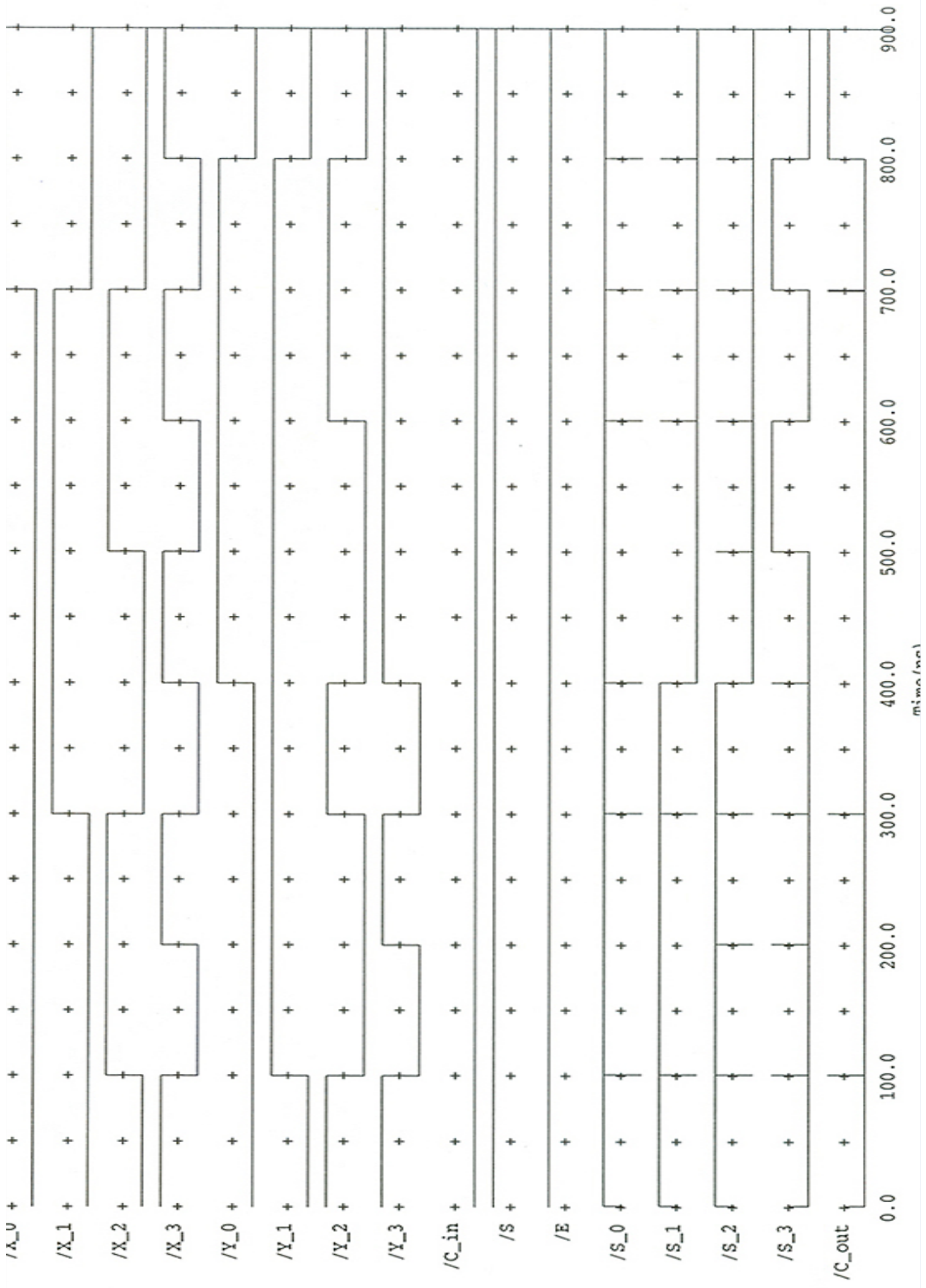

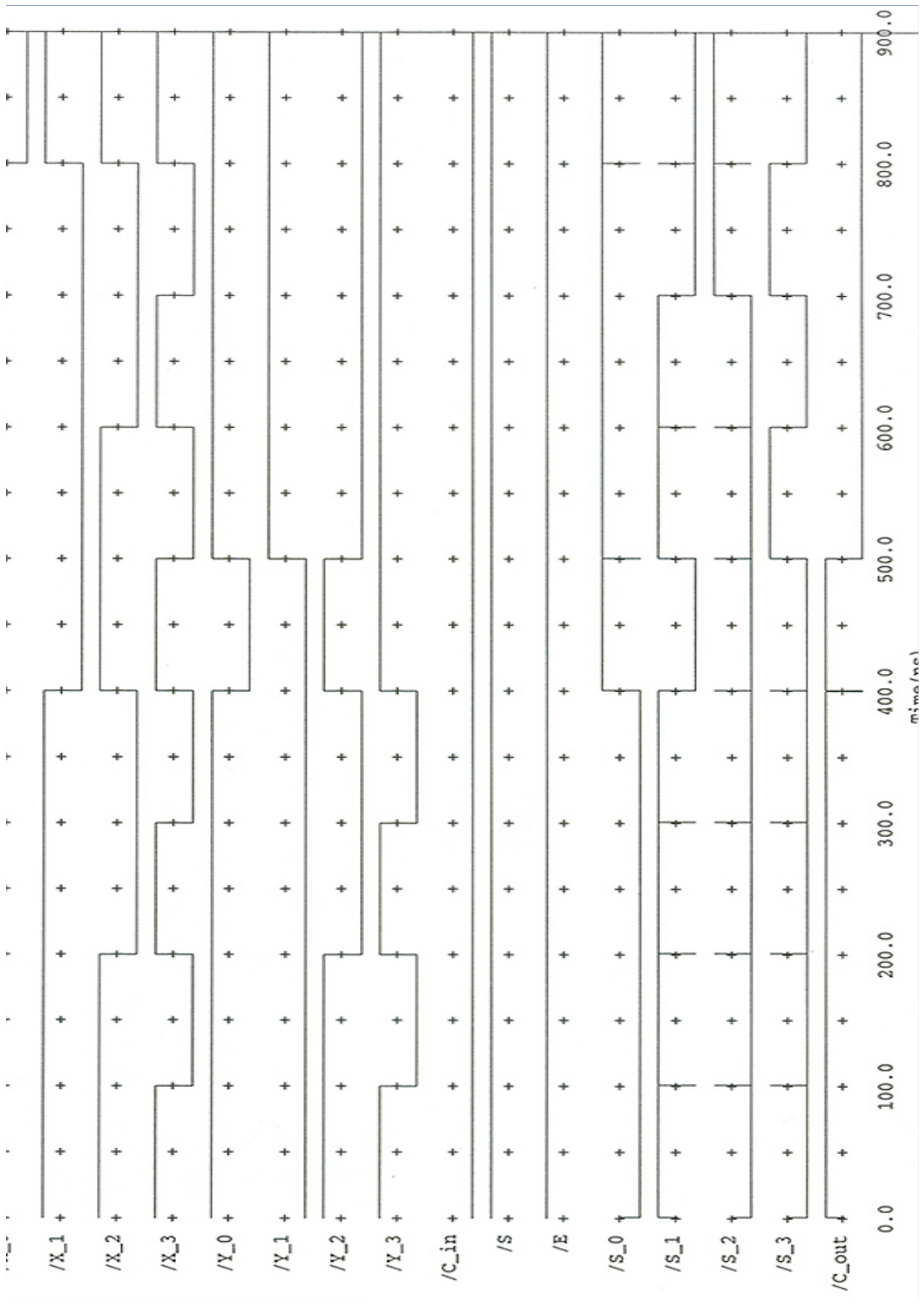

time/ns